

## Use of OP AMP as DA Converter (Digital – to – Analog Converter):


A device that produces an analog output voltage from a given digital input is called a digital-to-analog (DA) converter. We describe below two forms of DA converter using OP AMPs.

### (i) The Weighted-Resistor DA Converter:

To start with, we consider the conversion of a 4-bit digital data into an analog form. The decimal equivalent ( $N$ ) or analog form of a 4-bit digital data ( $B_3B_2B_1B_0$ ) is

$$N = 2^3B_3 + 2^2B_2 + 2^1B_1 + 2^0B_0 = \sum_{i=3}^0 2^i B_i \quad (B_i = 0 \text{ or } 1, i = 0, 1, 2, 3)$$

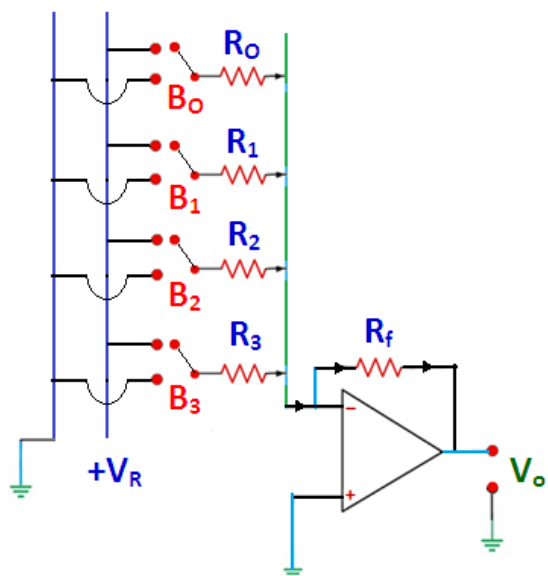where each bit of the data contributes to the final value with a weight  $2^i$  multiplied by the value of  $B_i$  ( $i = 0, 1, 2, 3$ ). Since  $B_i$  is either 0 or 1, the contribution is clearly zero or the bit weight. Here  $B_0$  is the least significant bit (LSB) and  $B_3$  is the most significant bit (MSB).



The conversion circuit is thus required to produce an output signal weighted according to the bit positions and to add them together. A basic 'Weighted Resistor' circuit for the conversion of a 4-bit digital data using an OP AMP is shown in figure. The logic voltages representing the individual bits  $B_3, B_2, B_1$  and  $B_0$  are applied to the resistors of the converter through switches. When the coefficient  $B_i$  is 1, the corresponding switch is closed, thus connecting a stabilized voltage source  $V_R$  to the converter.

When  $B_i$  is 0, the corresponding switch is connected to the ground. The resistors  $R_0, R_1, R_2$  and  $R_3$  in the circuit are weighted so that the successive resistors ratio is 2, i.e.  $\frac{R_0}{R_1} = \frac{R_1}{R_2} = \frac{R_2}{R_3} = 2$ , and each resistor is inversely proportional to the numerical significance of the appropriate binary bit. Thus, if  $R$  is any arbitrary resistance selected to suit the impedance level of the circuit, then

$$R_0 = \frac{R}{2^0} = R; R_1 = \frac{R}{2^1} = \frac{R}{2}; R_2 = \frac{R}{2^2} = \frac{R}{4}; \text{ and } R_3 = \frac{R}{2^3} = \frac{R}{8}.$$

The current  $i$  to the non-inverting input terminal is  $i = V_R \left( \frac{B_3}{R_3} + \frac{B_2}{R_2} + \frac{B_1}{R_1} + \frac{B_0}{R_0} \right)$

Substituting the values of  $R_0$ ,  $R_1$ ,  $R_2$ , and  $R_3$  we obtain

$$i = \frac{V_R}{R} (2^3 B_3 + 2^2 B_2 + 2^1 B_1 + 2^0 B_0)$$


Since  $G$  is a virtual ground, we have for the output voltage

$$V_0 = -iR_f = -\frac{V_R}{R} R_f (2^3 B_3 + 2^2 B_2 + 2^1 B_1 + 2^0 B_0)$$

Thus the output voltage is proportional to the numerical value or analog form of the binary input.

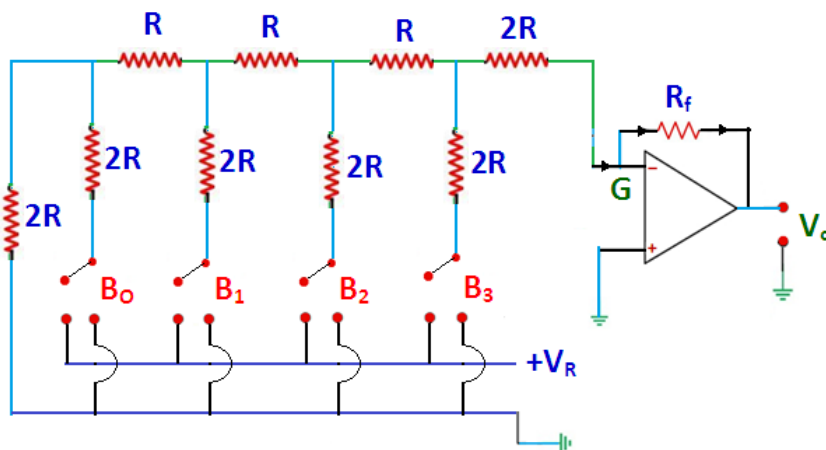
### (ii) The R-2R Ladder Converter:

A circuit of resistive R-2R ladder converter for a 4-bit digital data is shown in figure. To explain the operation of the circuit and to find the output voltage we have to find the net current flow  $i$  through the feedback resistance so that we get the output voltage of OP AMP as  $V_0 = -iR_f$ . This current flow  $i$  can be now obtained by applying the principle of superposition after finding each individual contribution for each applied voltage terminal in accordance with the input digital data. Again here we consider the conversion of input 4-bit digital data ( $B_3 B_2 B_1 B_0$ ) to its analog form as before.



By the principle of superposition, we now assume that the terminal  $B_0$  is connected to  $V_R$  and all other terminals namely,  $B_1$ ,  $B_2$  and  $B_3$  are connected to ground. The resulting resistive portion of the ladder is shown in figure. Applying **Thevenin's**

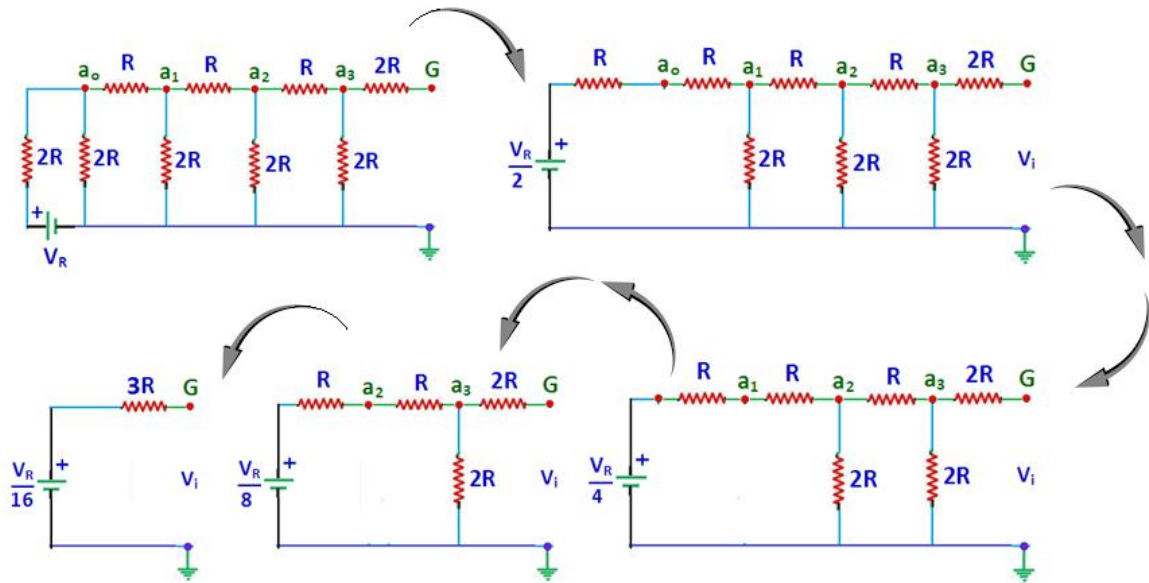**theorem** successively to the nodes  $a_0$ ,  $a_1$ ,  $a_2$  and  $a_3$  with respect to ground we obtain the equivalent Thevenin networks shown in figure. The final equivalent Thevenin source has a voltage of  $\frac{V_R}{16}$  in series with a resistance  $3R$  (as shown in figure)



Again if the terminal  $B_1$  in original figure is connected to the reference  $V_R$  and the terminals  $B_0, B_2$  and  $B_3$  are connected to ground, then it can also be shown in similar manner that the above procedure gives an equivalent simple network having the Thevenin voltage  $\frac{V_R}{8}$  in series with a resistance  $3R$  connected to the inverting input terminal of the OP AMP.

Similarly when the terminal  $B_2$  is connected to  $V_R$  and  $B_0, B_1$  and  $B_3$  be grounded, the corresponding Thevenin equivalent circuit has a voltage  $\frac{V_R}{4}$  in series with a resistance  $3R$ .

Lastly when the terminal  $B_3$  is connected to  $V_R$ , and  $B_0, B_1$  and  $B_2$  be switched to ground, the equivalent Thevenin source will consist of a voltage source  $\frac{V_R}{2}$  in series with a resistance  $3R$ .

The current  $i$  obtained by the principle of superposition is  $i = i_0 + i_1 + i_2 + i_3$

But usually we have  $i_0 = \frac{B_0(\frac{V_R}{16})}{3R}$ ,  $i_1 = \frac{B_1(\frac{V_R}{8})}{3R}$ ,  $i_2 = \frac{B_2(\frac{V_R}{4})}{3R}$ ,  $i_3 = \frac{B_3(\frac{V_R}{2})}{3R}$

Thus we get 
$$i = \frac{V_R}{3R} \left( \frac{B_0}{16} + \frac{B_1}{8} + \frac{B_2}{4} + \frac{B_3}{2} \right).$$

Since  $G$  is a virtual ground, we obtain for the output voltage of the OP AMP

$$V_0 = -iR_f = -\frac{R_f}{3R} V_R \left( \frac{B_0}{2^4} + \frac{B_1}{2^3} + \frac{B_2}{2^2} + \frac{B_3}{2^1} \right)$$

Here  $B_i = 1$  where the terminal is connected to  $V_R$ , and  $B_i = 0$  when the terminal is connected to ground ( $i = 0, 1, 2, 3$ ). Above equation can be rewritten as

$$V_0 = -\frac{R_f V_R}{48R} (2^3 B_3 + 2^2 B_2 + 2^1 B_1 + 2^0 B_0).$$

Clearly, the **output voltage** is proportional to the numerical value or **analog form** of the **digital input**. Thus digital to analog data conversion is made by this **R-2R** ladder network.

WWW.CTPhysics.org